



29th Annual
HANDS-ON
RELAY SCHOOL
 March 12 - 16, 2012



BREAKER FAILURE PROTECTION

Brent Carper, PE
 Protection & Integration Engineer
 brent.c@relayapplication.com



Relay Application Innovation, Inc.
Electric power system protection services, systems, and tools
 www.RelayApplication.com 509.334.9138

OUTLINE



- Protection System Failures and Breaker Failures
- BF Protection versus BF Relaying
- BF Relay Schemes and Logic
- Special BF Situations
- BF Setting Calculation Exercise
- Impacts from Changing Technology
- Testing and Maintenance of BF Schemes

Primary Reference:
 C37.119 -2005 IEEE Guide for Breaker Failure Protection of Power Circuit Breakers

PROTECTION FAILURE

Protection System Failures	Breaker Failures
<ul style="list-style-type: none"> ■ Relay failure ■ Settings failure ■ Control system failure ■ CT/PT failure ■ Battery system failure ■ Catastrophic control house failure (fire) 	<ul style="list-style-type: none"> ■ Fails to trip ■ Trips too slow ■ Fails to interrupt fault current ■ Fails to interrupt load current ■ Flashover when open ■ Fails to close ■ Auxiliary contact problems ■ Catastrophic failure

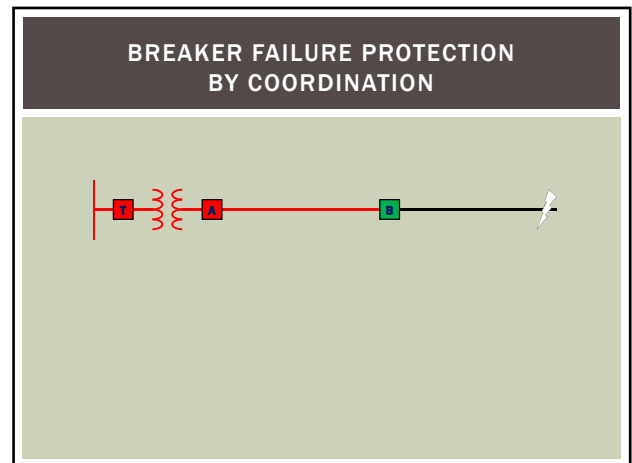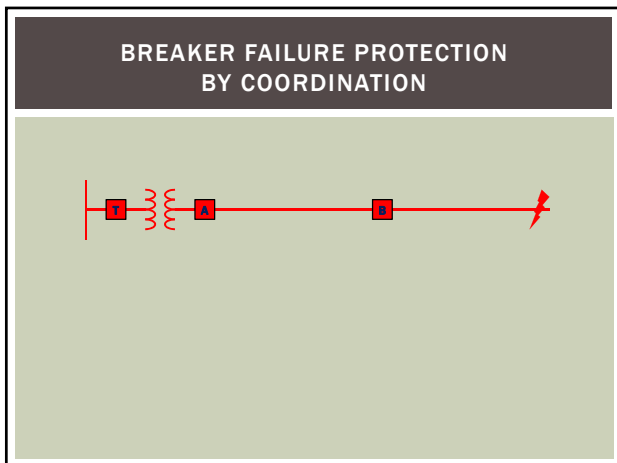Breaker Failure Protection versus Breaker Failure Relaying



BREAKER FAILURE PROTECTION BY COORDINATION

BREAKER FAILURE PROTECTION BY COORDINATION

Advantages:

- Simple – No extra equipment
- Simple – No risk of misoperation
- Ultimate protection. Covers ALL failures, not just Breaker Failure (failure of breaker, relay, settings, controls and wiring, battery, etc.)

Disadvantages:

- Slow
- May not be possible for the backup relaying at [A] to see all faults

Conclusions:

- Common practice for Distribution, but typically not sufficient for Transmission.
- There is “Breaker Fail Protection” even though there is not “Breaker Fail Relaying”.
- Breaker failure protection is built-in to good protection practices.

BREAKER FAILURE PROTECTION BY COORDINATION







[A] can probably back up [B] and see a minimum fault all the way at the end of the line. [M] may not be able to fully back up the feeder breakers for an end of line fault.

Example: Assume 200A load per feeder section, and 800A minimum fault current at the end of line. [A] has 400A max load and needs to pickup on an 800A fault. [M] has 1000A max load, so it cannot be set to pickup on an 800A fault.

IEEE EXAMPLE

IEEE EXAMPLE PROPER CLEARING


IEEE EXAMPLE BREAKER FAILURE

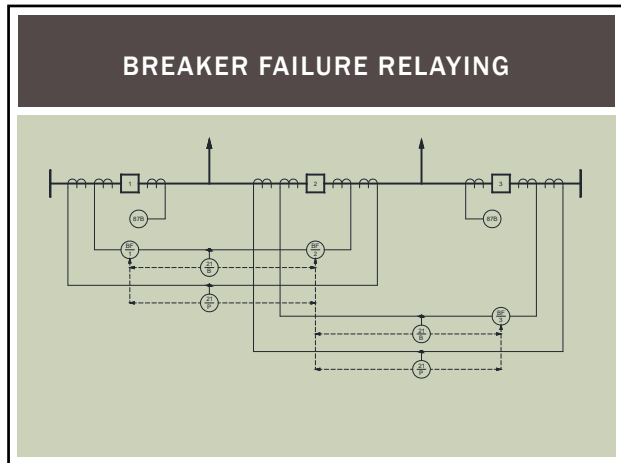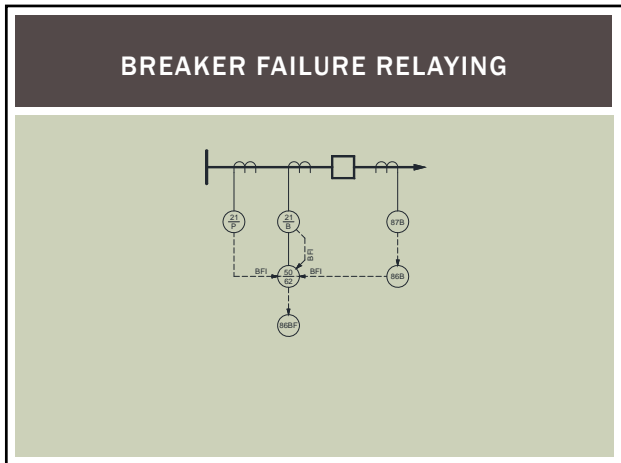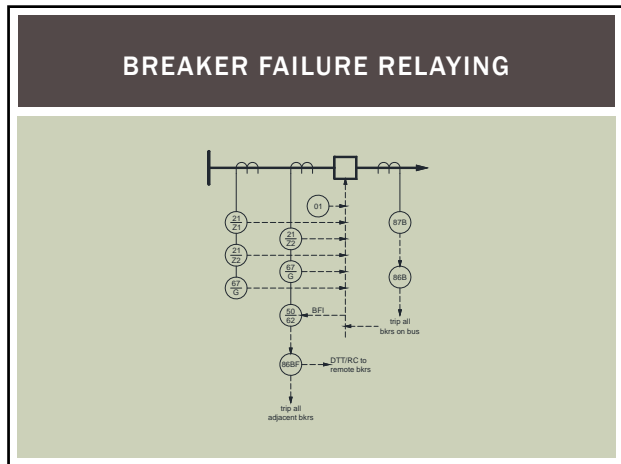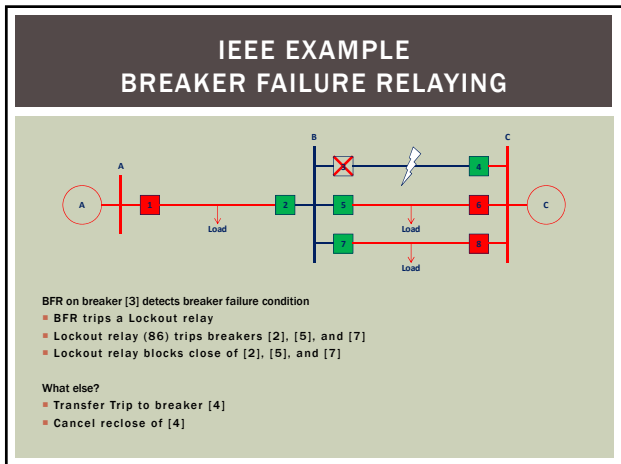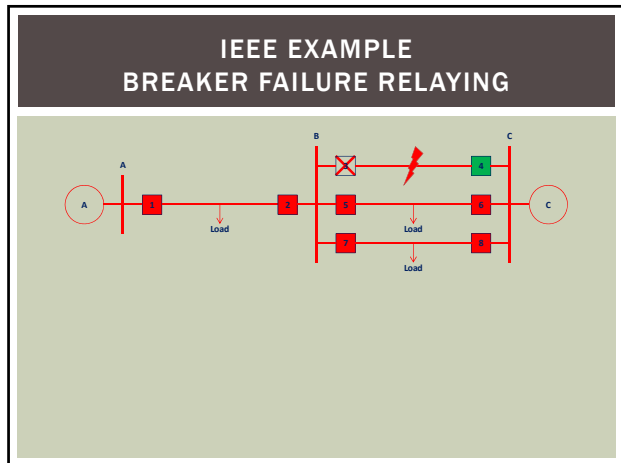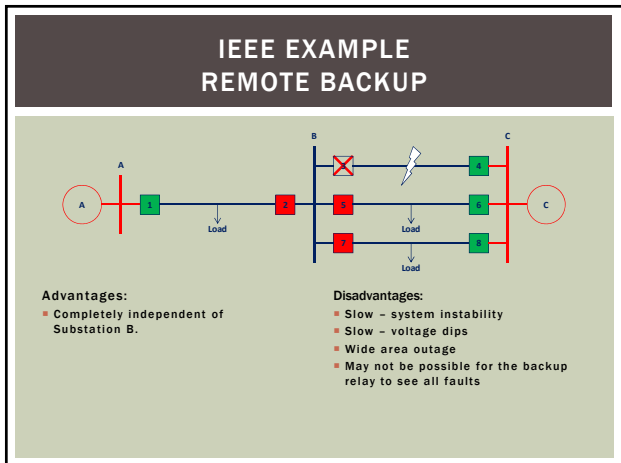

BREAKER FAILURE LOGIC

1. Basic Breaker Failure Scheme
2. 50BF Torque Control
3. Breaker Re-Trip Logic
4. BFI Control Timer
5. BFI Seal-In
6. Minimal Current Scheme
7. Timer Bypass Scheme
8. Dual Timer Scheme
9. Special Schemes


BASIC BREAKER FAILURE SCHEME

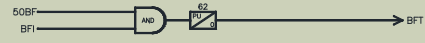

The diagram shows a logic circuit where two inputs, 50BF and BFI, are connected to an AND gate. The output of the AND gate is connected to a normally open contact labeled 62, which is then connected to the output BFT.


- Four Parts to a Breaker Failure Scheme:
 - Fault Detector (50) or other Failure Detectors
 - Initiator Circuit (BFI)
 - Logic and Timers (62)
 - Output Circuit (BFT)

50BF TORQUE CONTROL




The diagram shows a logic circuit where BFI is connected to a normally open contact labeled 62. This contact is connected to an AND gate. The output of the AND gate is connected to the output BFT. A normally open contact labeled 50BF is connected to the 62 contact, and a normally closed contact labeled ENABLE is connected to the 62 contact.

BREAKER RE-TRIP LOGIC

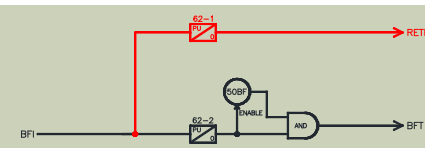


The diagram shows a logic circuit where BFI is connected to a normally open contact labeled 62-2. This contact is connected to an AND gate. The output of the AND gate is connected to the output BFT. A normally open contact labeled 50BF is connected to the 62-2 contact, and a normally closed contact labeled ENABLE is connected to the 62-2 contact. A normally open contact labeled 62-1 is connected to the output BFT, and a normally open contact labeled RETRIP is connected to the 62-1 contact.

BFI CONTROL TIMER

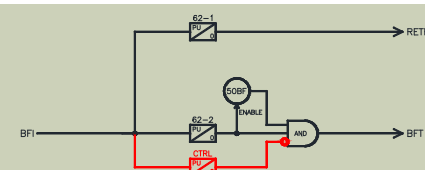


The diagram shows a logic circuit where BFI is connected to a normally open contact labeled 62-2. This contact is connected to an AND gate. The output of the AND gate is connected to the output BFT. A normally open contact labeled 50BF is connected to the 62-2 contact, and a normally closed contact labeled ENABLE is connected to the 62-2 contact. A normally open contact labeled 62-1 is connected to the output BFT, and a normally open contact labeled RETRIP is connected to the 62-1 contact. A normally open contact labeled CTBL is connected to the 62-2 contact, and a normally open contact labeled 62-3 is connected to the 62-2 contact.

BFI SEAL-IN



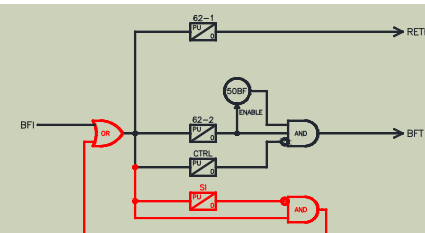






The diagram shows a logic circuit where BFI is connected to a normally open contact labeled 62-2. This contact is connected to an AND gate. The output of the AND gate is connected to the output BFT. A normally open contact labeled 50BF is connected to the 62-2 contact, and a normally closed contact labeled ENABLE is connected to the 62-2 contact. A normally open contact labeled 62-1 is connected to the output BFT, and a normally open contact labeled RETRIP is connected to the 62-1 contact. A normally open contact labeled CTBL is connected to the 62-2 contact, and a normally open contact labeled 62-3 is connected to the 62-2 contact. A normally open contact labeled 62-4 is connected to the output BFT, and a normally open contact labeled 62-5 is connected to the 62-4 contact.

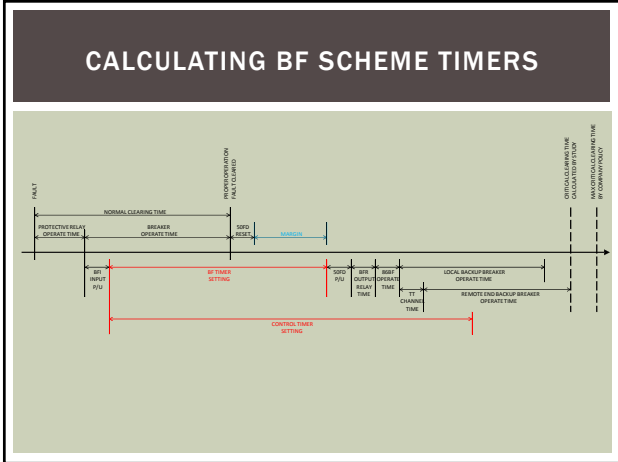

IMPACT OF CHANGING TECHNOLOGY

- **Digital Relay BF Protection: Faster, Better, Cheaper, More**
 - Solved transient stability problems previously unsolvable
 - Better protection against wide-area and cascading outages
 - Protect against all breaker failure modes, not just one or two
 - Can be more secure if designed well
- **Most utilities moving away from Stand-Alone BF Relays**
 - Some utilities (not many) are reversing the trend and going back to stand alone Breaker Failure Relays
 - Reduce **misoperations** "unscheduled maintenance tests"
 - Use longer maintenance cycles for BF protection systems

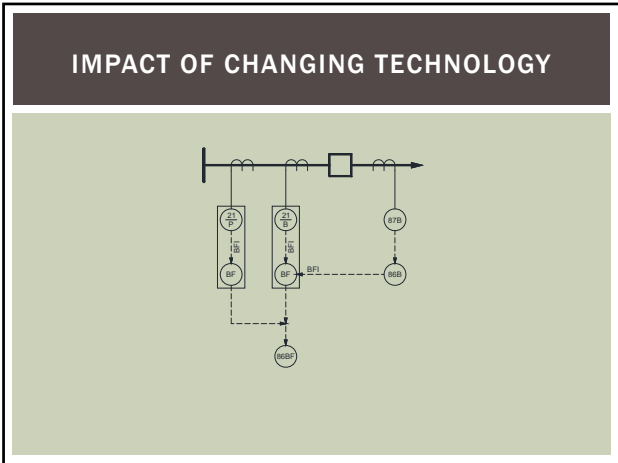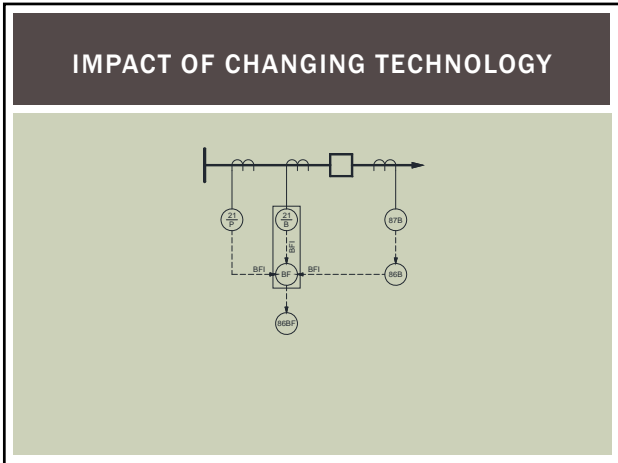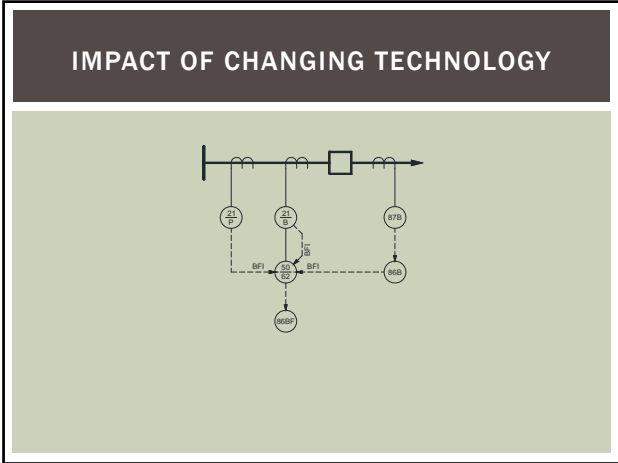

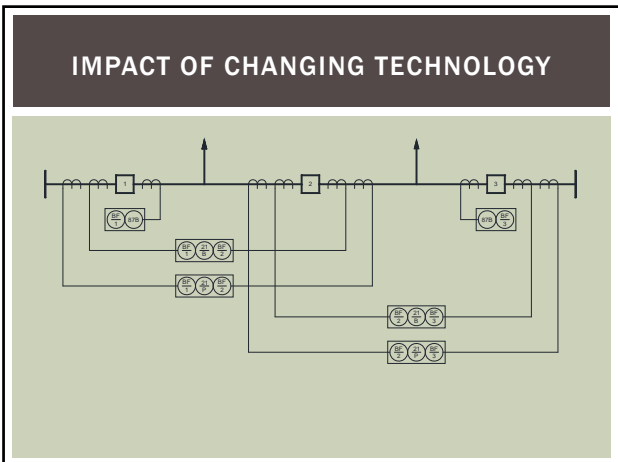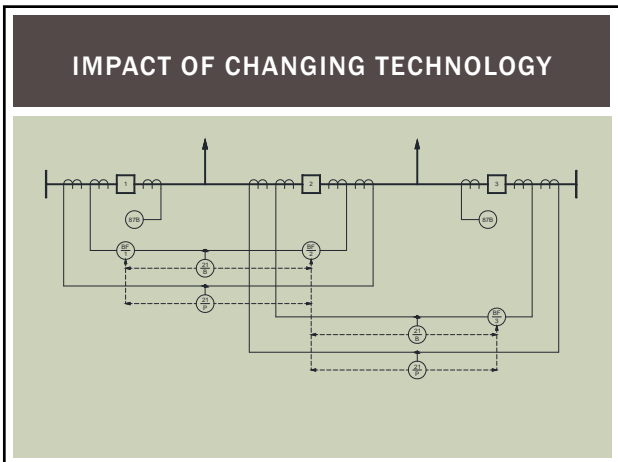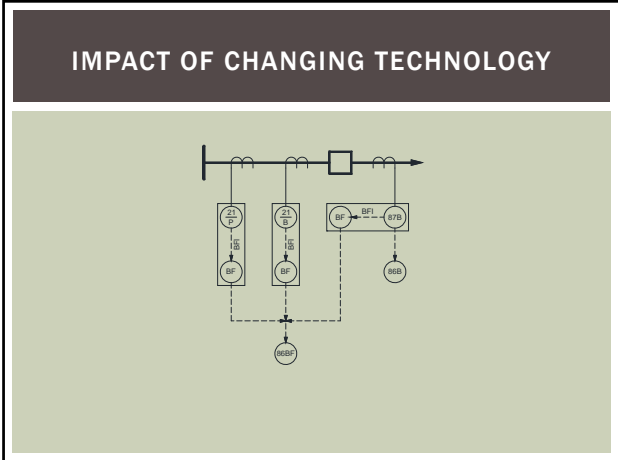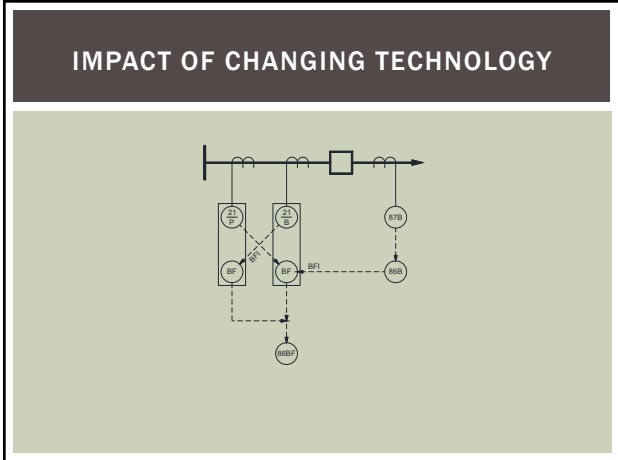

IMPACT OF CHANGING TECHNOLOGY

- **Digital Relay Timing and Logic**
 - Precise timing eliminates relay misoperations due to calibration drift
 - Precise timing and logic allows reducing "design margins"
- **Digital Relay I/O**
 - Sensitive BFI inputs (transients, DC grounds)
 - Solid state relay outputs (sneak circuits)
- **Digital Relay Protective Elements**
 - Used to be limited to a 50FD
 - Now we can use 50L and other sensitive detectors that may pick up a lot
 - *Solution: Consider using other elements to help add Security, not just Sensitivity (negative sequence, voltage elements, synch check and frequency elements, etc.)*

IMPACT OF CHANGING TECHNOLOGY

- **Challenges from Complexity**
 - Elaborate/exotic BF logic
 - Wide variety of BF schemes, even in the same model of relay at the same utility
 - May have more than one BF scheme in a single relay
 - May have more than one BF scheme for single breaker
 - *Solution: Engineering Standardization*
 - *Solution: Documentation (written setting descriptions, logic diagrams, and test plans)*
- **Challenges with Integrated BF**
 - May not be able to disable all BFI's
 - May not be able to disable all BFT's
 - Trend is to completely eliminate all hardwired BFT and lockout relays (IEC 61850)
 - *Solution: Design with test switch to relay input that disables the BFI and/or BFT. Especially important for BFTT or 61850.*

**TESTING AND MAINTENANCE
OF BREAKER FAILURE PROTECTION**

Challenges with BF Protection

- Difficult to test intentionally
- Easy to test unintentionally

**TESTING AND MAINTENANCE
OF BREAKER FAILURE PROTECTION**

**There is a difference between testing the BF Relay
and testing the BF Relaying System**

- Many utilities perform maintenance testing of the BF Relay, but are not testing the entire Breaker Failure Protection System.
- Good maintenance practices (and NERC compliance requirements) are to test the Protection System:
 - Maintenance program for the BF Relay
 - Maintenance program for CT's/PT's
 - Maintenance program for the Battery and DC system
 - Maintenance of the BFR Protection System must include:
 - Rolling lockout relays and tripping breakers
 - Best practice: simultaneous functional test (clear the bus)

Brent Carper, PE
Protection & Integration Engineer
brent.c@relayapplication.com
509.334.9138



Electric power system protection services, systems, and tools
www.RelayApplication.com 509.334.9138